



Universidade Federal do Ceará
Instituto de Tecnologia
Departamento de Engenharia Elétrica

Circuitos Elétricos

Capítulo 4 C – Técnicas de Análise de Circuitos



Prof. Fabrício Nogueira



Método das Correntes de Malha

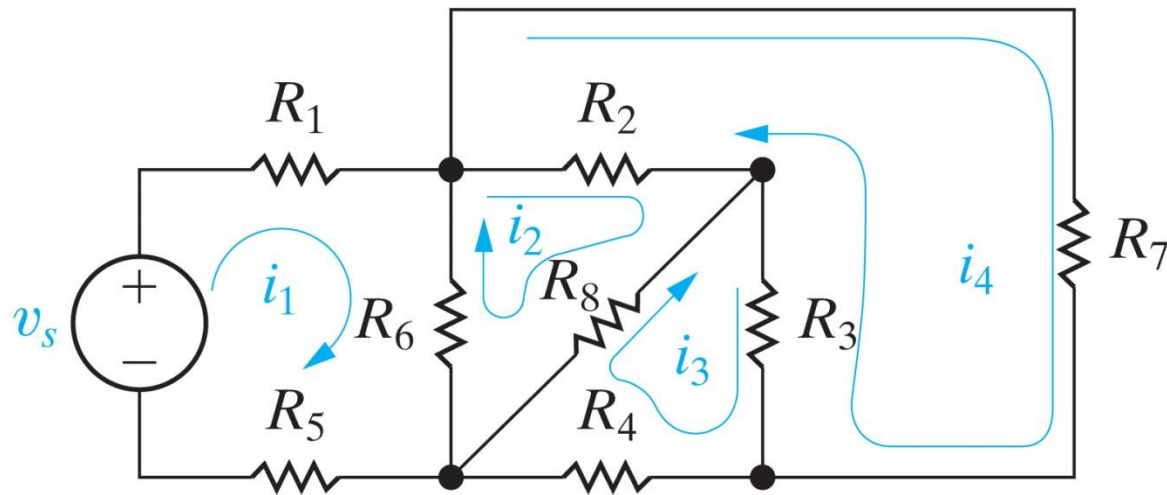


Figure: 04-18

Copyright © 2008 Pearson Prentice Hall, Inc.



Método das Correntes de Malha

⚡ Aplicando as Leis de Kirchhoff:

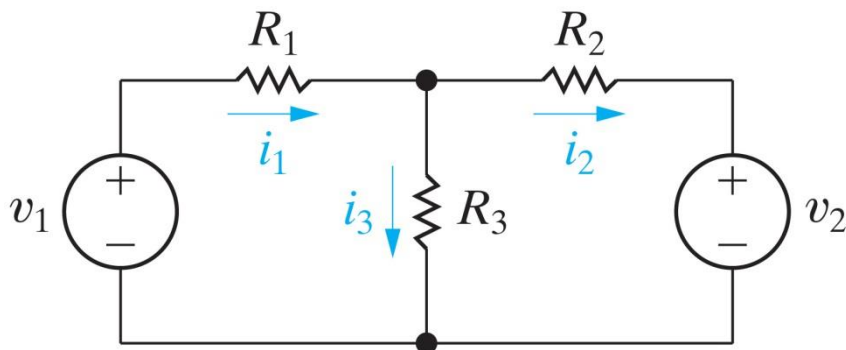


Figure: 04-19

Copyright © 2008 Pearson Prentice Hall, Inc.

$$\begin{aligned}i_1 &= i_2 + i_3, \\v_1 &= i_1 R_1 + i_3 R_3, \\-v_2 &= i_2 R_2 - i_3 R_3.\end{aligned}$$



$$\begin{aligned}v_1 &= i_1(R_1 + R_3) - i_2 R_3, \\-v_2 &= -i_1 R_3 + i_2(R_2 + R_3).\end{aligned}$$



Método das Correntes de Malha

⚡ Aplicando as Leis de Kirchhoff:

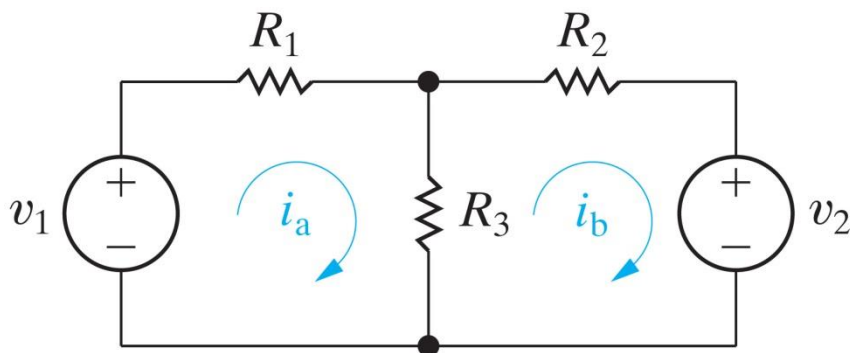


Figure: 04-20

Copyright © 2008 Pearson Prentice Hall, Inc.

$$\begin{aligned} v_1 &= i_a R_1 + (i_a - i_b) R_3, \\ -v_2 &= (i_b - i_a) R_3 + i_b R_2. \end{aligned}$$



$$\begin{aligned} i_1 &= i_a, \\ i_2 &= i_b, \\ i_3 &= i_a - i_b. \end{aligned}$$

$$\begin{aligned} v_1 &= i_a (R_1 + R_3) - i_b R_3, \\ -v_2 &= -i_a R_3 + i_b (R_2 + R_3). \end{aligned}$$



Método das Correntes de Malha

⚡ Exemplo:

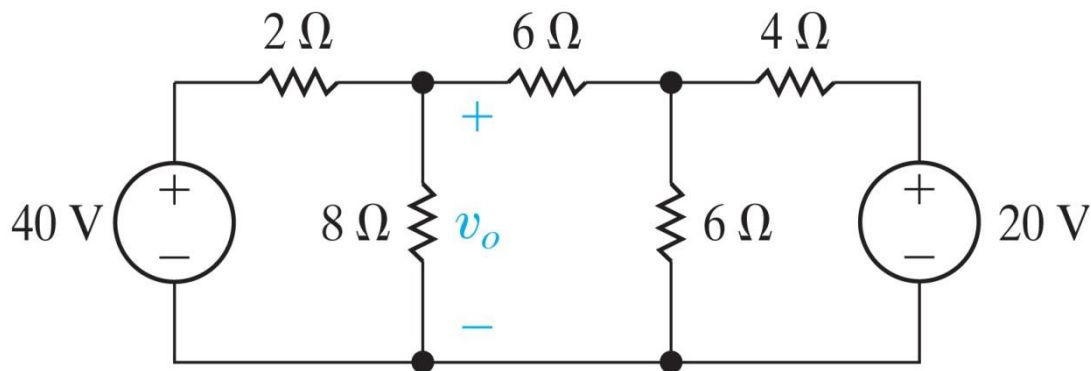


Figure: 04-21Ex4.4

Copyright © 2008 Pearson Prentice Hall, Inc.

- Use the mesh-current method to determine the power associated with each voltage source in the circuit shown in Fig. 4.21.
- Calculate the voltage v_o across the $8\ \Omega$ resistor.



Método das Correntes de Malha

⚡ Example:

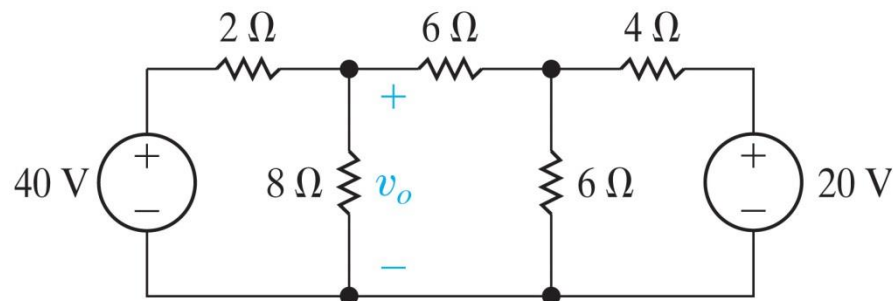


Figure: 04-21Ex4.4

2008 Pearson Prentice Hall, Inc.

$$-40 + 2i_a + 8(i_a - i_b) = 0,$$

$$8(i_b - i_a) + 6i_b + 6(i_b - i_c) = 0,$$

$$6(i_c - i_b) + 4i_c + 20 = 0.$$

$$10i_a - 8i_b + 0i_c = 40;$$

$$-8i_a + 20i_b - 6i_c = 0;$$

$$0i_a - 6i_b + 10i_c = -20.$$



$$i_a = 5.6 \text{ A},$$

$$i_b = 2.0 \text{ A},$$

$$i_c = -0.80 \text{ A}.$$

$$p_{40V} = -40i_a = -224 \text{ W}.$$

$$p_{20V} = 20i_c = -16 \text{ W}.$$

$$v_o = 8(i_a - i_b) = 8(3.6) = 28.8 \text{ V}.$$



Método das Correntes de Malha

⚡ Assessment problem:

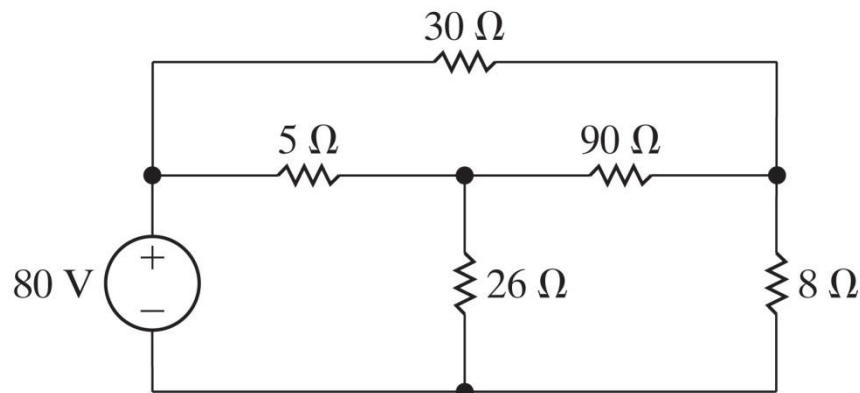


Figure: 04-22-01AO2-4.7

Copyright © 2008 Pearson Prentice Hall, Inc.


- 4.7** Use the mesh-current method to find (a) the power delivered by the 80 V source to the circuit shown and (b) the power dissipated in the 8 Ω resistor.

Answer: (a) 400 W;
(b) 50 W.



Método das Correntes de Malha

⚡ Solution:

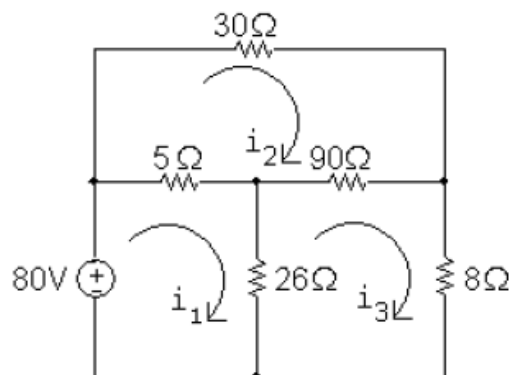

$$-80 + 5(i_1 - i_2) + 26(i_1 - i_3) = 0$$

$$30i_2 + 90(i_2 - i_3) + 5(i_2 - i_1) = 0$$

$$8i_3 + 26(i_3 - i_1) + 90(i_3 - i_2) = 0$$



$$31i_1 - 5i_2 - 26i_3 = 80$$

$$-5i_1 + 125i_2 - 90i_3 = 0$$

$$-26i_1 - 90i_2 + 124i_3 = 0$$

$$i_1 = 5 \text{ A}; \quad i_2 = 2 \text{ A}; \quad i_3 = 2.5 \text{ A}$$

$$p_{8\Omega} = (8)i_3^2 = 8(2.5)^2 = 50 \text{ W}$$

$$p_{80V} = -(80)i_1 = -(80)(5) = -400 \text{ W}$$



Método das Correntes de Malha

Use the mesh-current method of circuit analysis to determine the power dissipated in the $4\ \Omega$ resistor in the circuit shown in Fig. 4.23.

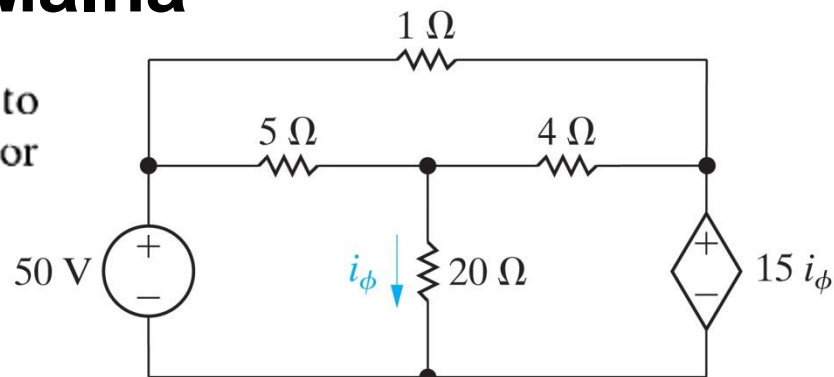


Figure: 04-23Ex4.5

Copyright © 2008 Pearson Prentice Hall, Inc.

$$50 = 5(i_1 - i_2) + 20(i_1 - i_3),$$

$$0 = 5(i_2 - i_1) + 1i_2 + 4(i_2 - i_3),$$

$$0 = 20(i_3 - i_1) + 4(i_3 - i_2) + 15i_\phi.$$

$$i_\phi = i_1 - i_3,$$



$$50 = 25i_1 - 5i_2 - 20i_3,$$

$$0 = -5i_1 + 10i_2 - 4i_3,$$

$$0 = -5i_1 - 4i_2 + 9i_3.$$

$$i_2 = 26\text{ A},$$

$$i_3 = 28\text{ A}.$$

$$p_{4\Omega} = (i_3 - i_2)^2(4) = (2)^2(4) = 16\text{ W}.$$



Caso especial: Supermalha

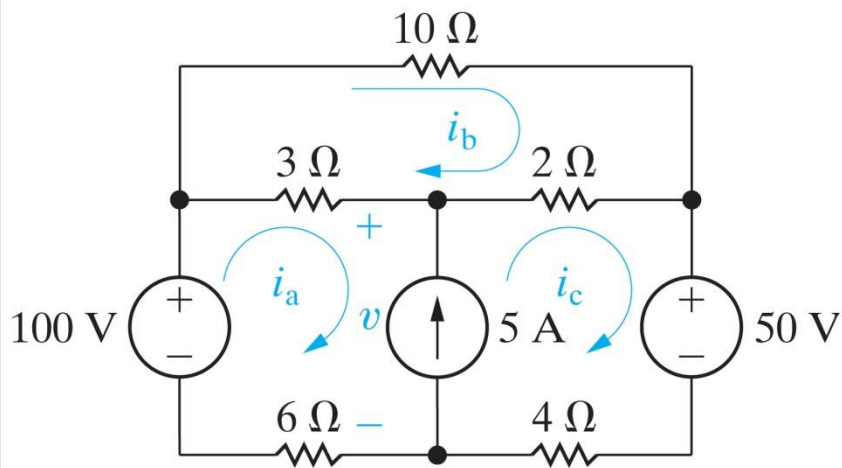


Figure: 04-25

Copyright © 2008 Pearson Prentice Hall, Inc.

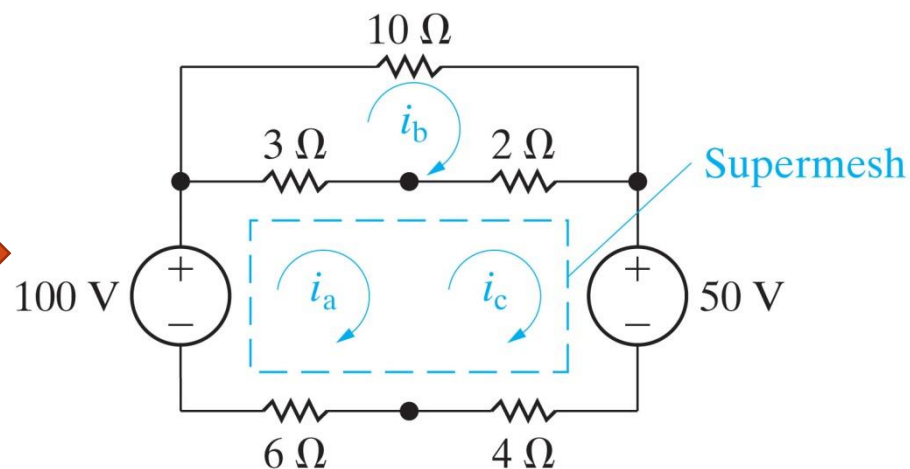


Figure: 04-26

Copyright © 2008 Pearson Prentice Hall, Inc.

Malha a) $100 = 3(i_a - i_b) + v + 6i_a,$

Malha c) $-50 = 4i_c - v + 2(i_c - i_b).$

$50 = 9i_a - 5i_b + 6i_c.$

Malha b)


$-100 + 3(i_a - i_b) + 2(i_c - i_b) + 50 + 4i_c + 6i_a = 0,$

$50 = 9i_a - 5i_b + 6i_c.$



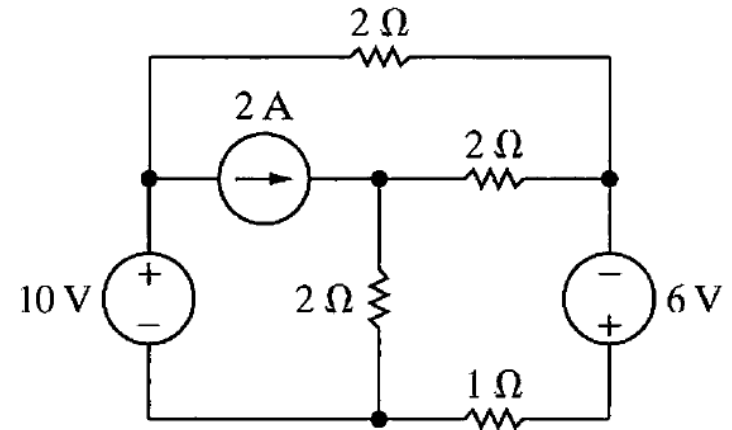Exercício

Use the mesh-current method to find the power dissipated in the $1\ \Omega$ resistor in the circuit shown.




Answer: 36 W.



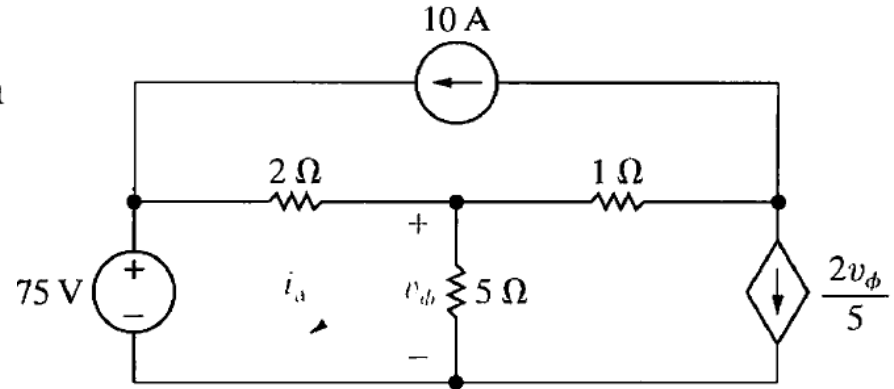Exercício

Use the mesh-current method to find the mesh current i_a in the circuit shown.



Answer: 15 A.



Referências Bibliográficas:

Nilsson, J.W. e Riedel, S.A., Circuitos Elétricos, 8^a Edição, Pearson Prentice Hall, São Paulo, 2009.

Svoboda, J.A. and Dorf, R.C., Introduction to Electric Circuits, 9th edition, Wiley, 2011.